

STEP1: Determine what type of the circuit is(refer the tree)



STEP2: Chunk the complex circuit to small function unit



STEP3: Analysis each unit, expressed it(based on 5 methods) if necessary



STEP4: Join all the units into a large scale

Procedure of Circuit Analysis